

Important MCQs of DLD

By: Prof. Fazal Rehman Shamil Last Modified: April 19, 2020

Important MCQs of DLD

1. Why we use demultiplexer?

- A. Route the data from a single input to one of many outputs
- B. Select data from several inputs and route it to a single output
- C. Perform [serial to parallel](#) conversion
- D. Both a and b

Answer - Click Here:

D

2. Which is an [example of synchronous](#) inputs?

- A. Preset input (PRE)
- B. EN input
- C. J-K input
- D. Clear Input (CLR)

Answer - Click Here:

C

3. Which one is the Second step of making [transition table](#)?

- A. determining feedback loop
- B. designating output of loops
- C. deriving functions of Y
- D. plotting

Answer - Click Here:

B

4. We can be imagined that an or gate is look like _____

- A. Switches connected in parallel
- B. Switches connected in series
- C. MOS transistors connected in series
- D. None of these

Answer - Click Here:

A

5. The change from a current state to the next state is determined by

- A. Previous state and outputs
- B. Current state and outputs
- C. Current state and the inputs
- D. Previous state and inputs

Answer - Click Here:

C

Search

MCQS

MCQs – Database Systems
MCQs – Computer Network
MCQs Data Structures
MCQs-Computer Science Basics
MCQs – Computer Science
MCQs – English
MCQs – Biology
MCQs – Everyday Science
MCQs – General Knowledge
MCQs – Islamic studies
MCQs – Maths
MCQs – Physics
MCQs – Geography
MCQs – Economics
MCQs – Statistics
MCQs – Programming C Plus Plus
MCQs – Ethics
MCQs – Visual Programming
MCQs – Management Sciences
MCQs – Social Studies
MCQs – Communication skills
MCQs – General
Engineering MCQs Homepage
Psychology MCQs
Philosophy Of Science

6. Each gate take time for delay _____

- A. 2 to 10 ns
- B. 3 to 10 ns
- C. 1 to 5 ns
- D. 3 to 5 ns

Answer - Click Here:

A

7. In Which combination of gates the arbitrary Boolean function is not possible?

- A. OR gates and exclusive OR gate only
- B. [NAND gates](#) only
- C. OR gates and NOT gates only
- D. OR gates and AND gates only

Answer - Click Here:

D

8. Which one of the following is used to simplify the circuit that determines the next state?

- A. [State diagram](#)
- B. State assignment
- C. State reduction
- D. Next state table

Answer - Click Here:

A

9. When both inputs are _____ then NAND latch works.

- A. inverted
- B. 0
- C. 1
- D. don't cares

Answer - Click Here:

C

10. _____ adders are needed to construct an m-bit parallel adder.

- A. m+1
- B. m-1
- C. m
- D. m/2

Answer - Click Here:

B

11. _____ is converted by a multiplexer with a register circuit.

- A. Serial data to serial
- B. Serial data to parallel
- C. Parallel data to serial

D. Parallel data to parallel

Answer - Click Here:

C

12. changing in input more than one state is called _____

A. undefined condition

B. ideal condition

C. reset condition

D. [race condition](#)

Answer - Click Here:

D



Prof. Fazal Rehman Shamil

CEO @ **T4Tutorials.com**

I welcome to all of you if you want to discuss about any topic. Researchers, teachers and students are allowed to use the content for non commercial offline purpose. Further, You must use the reference of the website, if you want to use the partial content for research purpose.